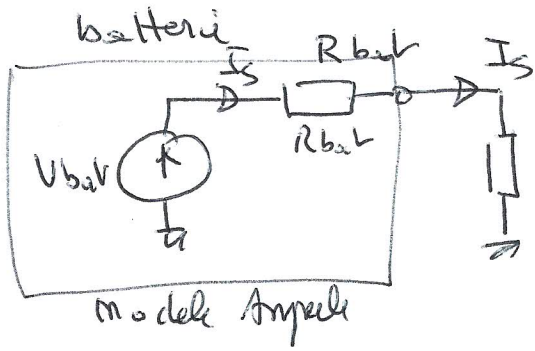



Correction Problème 1 ex 1



problème batterie branchée sur ampoule 12v 24W



$R_c \approx$ Ampoule

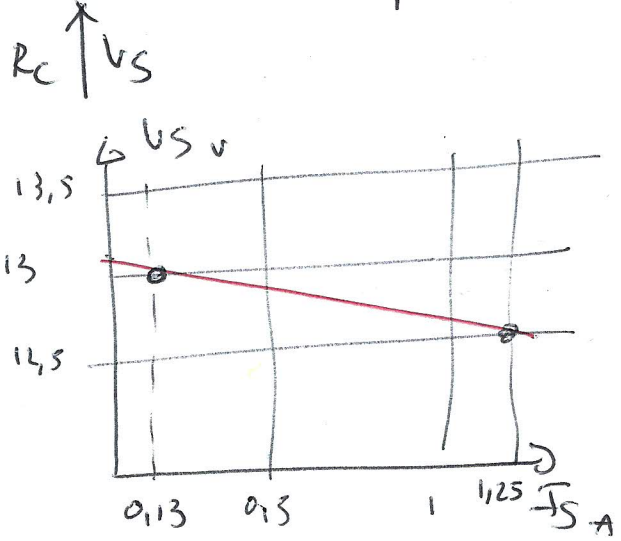

Q₁) Calcul R_{bat}

Rappel

$$V_S = V_{bat} - R_{bat} I_S$$

$$\frac{dV_S}{dI_S} = -R_{bat} = \frac{y_2 - y_1}{x_2 - x_1}$$

si $R_c = 100 \Omega$ $V_S = 13V$ $I = \frac{U}{R} = 0,13$

si $R_c = 10 \Omega$ $V_S = 12,5$ $I = 1,2 A$

$$-R_{bat} = \frac{dV_S}{dI_S} = \frac{12,5 - 13}{1,25 - 0,13} = \frac{-0,5}{1,12} = -R_{bat} = -0,5 \Rightarrow R_{bat} = 0,5 \Omega$$

Calcul V_{bat}

avec 100Ω $V_S = V_{bat} - 0,5 \times 0,13$

$$V_{bat} = 13V + (0,5 \times 0,13) = 13,05 V$$

$$\approx 0,5 \times 0,1 = 0,05$$


Q₂) Résistance Ampoule

$$P = \frac{U^2}{R} \quad \frac{U^2}{P} = R$$

$U = 12$
 $P = 24$

$$\frac{12 \times 12}{2 \times 12} = 6 \Omega$$

Q₃) quel sera V_S

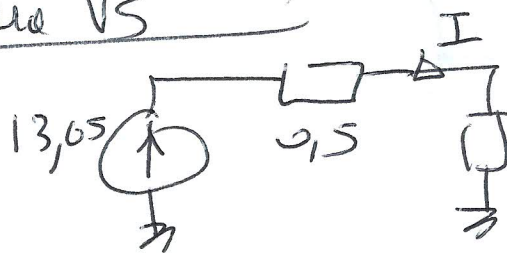

$$V_S = I R_c$$

$$I = \frac{13,05}{0,5 + 6}$$

$$V_S = 13,05 \times \frac{6}{0,5 + 6} \text{ ok}$$

$V_S = 12,5 V$ environ